

---

# 4X2 ADDITIVE MULTIPLY MODULE

---

Submitted by: Suhas Niranjana Yelluru [31371564]



PROF. TIMOTHY STEELE

NJIT  
ECE 689

## Table of Contents

<b>STRUCTURE OF PROJECT:</b> .....	<b>2</b>
1. Designing a single 4x2 AMM:.....	2
2. Two Latch: for all 3 downto 2 outputs on $X_L \times Y_{10}, X_L \times Y_{32}, X_L \times Y_{54}, X_L \times Y_{76}$ .....	4
3. Four Latch: for all 5 downto 2 outputs on $X_H \times Y_{10}, X_H \times Y_{32}, X_H \times Y_{54}, X_H \times Y_{76}$ .....	4
4. Calling all the above components to make an 8x8 multiplication:.....	5
<b>TESTBENCH</b> .....	<b>7</b>
<b>Results and Discussion:</b> .....	<b>8</b>
1. Elaborated Design: .....	8
2. Project Summary:.....	9
3. Outputs:.....	10
<b>POST BEHAVIORAL SYNTHESIS:</b> .....	<b>11</b>

## Table of Figures

<b>FIGURE 1: 4x2 AMM</b> .....	<b>3</b>
<b>FIGURE 2: USING 4x2 AMM'S FOR 8x8 MULTIPLICATION</b> .....	<b>4</b>
<b>FIGURE 3: AMM</b> .....	<b>8</b>
<b>FIGURE 4: TWO LATCH</b> .....	<b>8</b>
<b>FIGURE 5: FOUR LATCH</b> .....	<b>8</b>
<b>FIGURE 6: 8x8 MULTIPLICATION USING 8, 4x2 AMM'S</b> .....	<b>8</b>
<b>FIGURE 7: PROJECT SUMMARY</b> .....	<b>9</b>
<b>FIGURE 8: RESOURCE UTILIZATION</b> .....	<b>9</b>
<b>FIGURE 9: NUMBER OF LUT'S, IO'S FF'S ETC USED</b> .....	<b>9</b>
<b>FIGURE 10: EXAMPLE OUTPUT#1</b> .....	<b>10</b>
<b>FIGURE 11: EXAMPLE OUTPUT#2</b> .....	<b>10</b>
<b>FIGURE 12: SCHEMATIC FOR AMM USING MENTOR GRAPHICS TOOLKIT</b> .....	<b>11</b>
<b>FIGURE 13: SCHEMATIC FOR 8x8 PIPELINED MULTIPLIER USING 4x2 AMM'S</b> .....	<b>11</b>
<b>FIGURE 14: PAD FRAME FOR AMM</b> .....	<b>12</b>
<b>FIGURE 15: LAYOUT OF TWO LATCH</b> .....	<b>12</b>
<b>FIGURE 16: SCHEMATIC OF FOUR LATCH</b> .....	<b>13</b>
<b>FIGURE 17: LAYOUT OF FOUR LATCH</b> .....	<b>13</b>

## STRUCTURE OF PROJECT:

---

### 1. Designing a single 4x2 AMM:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity amm_module is
    Port ( clk : in STD_LOGIC;
          a : in STD_LOGIC_VECTOR (3 downto 0);
          b : in STD_LOGIC_VECTOR (1 downto 0);
          c : in STD_LOGIC_VECTOR (3 downto 0);
          d : in STD_LOGIC_VECTOR (1 downto 0);
          p : out STD_LOGIC_VECTOR (5 downto 0));
end amm_module;

architecture Behavioral of amm_module is
--signal clk : STD_LOGIC;
signal and00 : STD_LOGIC;
signal and10 : STD_LOGIC;
signal and20 : STD_LOGIC;
signal and30 : STD_LOGIC;
signal and01 : STD_LOGIC;
signal and11 : STD_LOGIC;
signal and21 : STD_LOGIC;
signal and31 : STD_LOGIC;

signal fa1c : STD_LOGIC;
signal fa2s : STD_LOGIC;
signal fa2c : STD_LOGIC;
signal fa3s : STD_LOGIC;
signal fa3c : STD_LOGIC;
signal fa4s : STD_LOGIC;
signal fa4c : STD_LOGIC;
signal fa5c : STD_LOGIC;
signal fa6c : STD_LOGIC;
signal fa7c : STD_LOGIC;

begin
    process(clk)
        begin
            if rising_edge(clk) then

                --AND Products
                and00 <= a(0) AND b(0);
                and10 <= a(1) AND b(0);
                and20 <= a(2) AND b(0);
                and30 <= a(3) AND b(0);
                and01 <= a(0) AND b(1);
                and11 <= a(1) AND b(1);
                and21 <= a(2) AND b(1);
                and31 <= a(3) AND b(1);

                --FULLADDER-1
                fa1c <= (c(0) AND and00) OR (d(0) AND and00) OR (c(1) AND d(0));
                p(0) <= c(0) XOR and00 XOR d(0);

                --FULLADDER-2
                fa2s <= and10 XOR and01 XOR c(1);
                fa2c <= (and10 AND and01) OR (and10 AND c(1)) OR (c(1) AND and01);

                --FULLADDER-3
                fa3s <= and20 XOR and11 XOR c(2);
                fa3c <= (and20 AND and11) OR (and20 AND c(2)) OR (c(2) AND and11);
```

```

--FULLADDER-4
fa4s <= and30 XOR and21 XOR c(3);
fa4c <= (and30 AND and21) OR (and30 AND c(3)) OR (c(3) AND and21);

--FULLADDER-5
p(1) <= fa1c XOR d(1) XOR fa2s;
fa5c <= (fa1c AND d(1)) OR (fa1c AND fa2s) OR (d(1) AND fa2s);

--FULLADDER-6
p(2) <= fa5c XOR fa2c XOR fa3s;
fa6c <= (fa5c AND fa2c) OR (fa5c AND fa3s) OR (fa3s AND fa2c);

--FULLADDER-7
p(3) <= fa3c XOR fa4s XOR fa6c;
fa7c <= (fa3c AND fa4s) OR (fa3c AND fa6c) OR (fa4s AND fa6c);

--FULLADDER-8
p(4) <= and31 XOR fa4c XOR fa7c;
p(5) <= (fa4c AND fa7c) OR (fa4c AND and31) OR (fa7c AND and31);

end if;
end process;
end Behavioral;

```

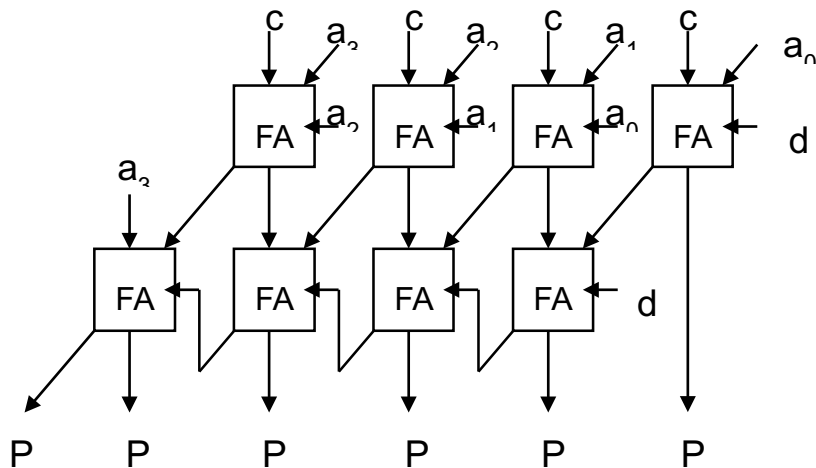


Figure 1: 4x2 AMM

In order to make the operation pipelined, we have to introduce latches for the outputs from AMM1 for the 3<sup>rd</sup> and 2<sup>nd</sup> bit, along with a latch for AMM2 for the 5<sup>th</sup> to 2<sup>nd</sup> bits.

This is because, these inputs need only one clock to be generated, however, the remaining inputs to the future AMMs would not have been generated.

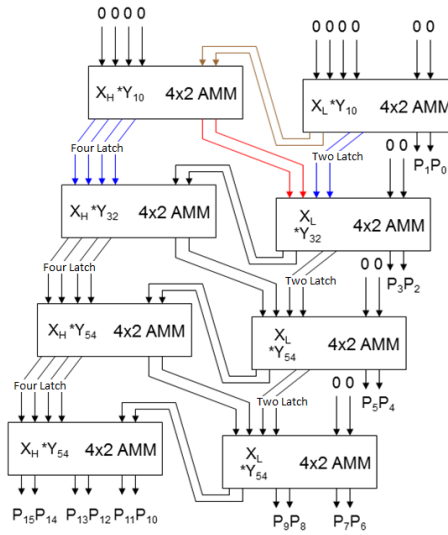


Figure 2: Using 4x2 AMM's for 8x8 multiplication

## 2. Two Latch: for all 3 downto 2 outputs on $X_L \times Y_{10}$ , $X_L \times Y_{32}$ , $X_L \times Y_{54}$ , $X_L \times Y_{76}$

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity twolatch is
    Port ( clk : in std_logic;
          p23 : in std_logic_vector(1 downto 0) := "00";
          o23 : out std_logic_vector(1 downto 0) := "00"
    );
end twolatch;

architecture Behavioral of twolatch is
    type t_mem is array(natural range <>) of std_logic_vector(1 downto 0);
    signal mem : t_mem(0 to 1) := (others => "00");
begin
    process(clk)
    begin
        if rising_edge(Clk) then
            o23 <= mem(1);
            --mem(1) <= mem(0);
            mem(1) <= p23;
        end if;
    end process;
end Behavioral;

```

## 3. Four Latch: for all 5 downto 2 outputs on $X_H \times Y_{10}$ , $X_H \times Y_{32}$ , $X_H \times Y_{54}$ , $X_H \times Y_{76}$

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity fourlatch is
    Port ( clk : in STD_LOGIC;
          p23 : in STD_LOGIC_VECTOR(3 downto 0) := "0000";
          o23 : out STD_LOGIC_VECTOR(3 downto 0) := "0000");
end fourlatch;

architecture Behavioral of fourlatch is
    type t_mem is array(natural range <>) of std_logic_vector(3 downto 0);
    signal mem : t_mem(0 to 1) := (others => "0000");

```

```

begin
  process (clk)
  begin
    if rising_edge(clk) then
      o23 <= mem(1);
      --mem(1) <= mem(0);
      mem(1) <= p23;
    end if;
  end process;
end Behavioral;

```

#### 4. Calling all the above components to make an 8x8 multiplication:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity ece689_proj is
  Port ( clk : in STD_LOGIC;
        a : in STD_LOGIC_VECTOR (7 downto 0);
        b : in STD_LOGIC_VECTOR (7 downto 0);
        p : out STD_LOGIC_VECTOR (15 downto 0));
end ece689_proj;

architecture Behavioral of ece689_proj is

  signal a1 : STD_LOGIC_VECTOR (3 downto 0);
  signal a2 : STD_LOGIC_VECTOR (3 downto 0);

  signal b1 : STD_LOGIC_VECTOR (1 downto 0);
  signal b2 : STD_LOGIC_VECTOR (1 downto 0);
  signal b3 : STD_LOGIC_VECTOR (1 downto 0);
  signal b4 : STD_LOGIC_VECTOR (1 downto 0);

  signal c : STD_LOGIC_VECTOR (3 downto 0) := "0000";
  signal d : STD_LOGIC_VECTOR (1 downto 0) := "00";

  --two latch outputs
  signal q1 : STD_LOGIC_VECTOR (1 downto 0);
  signal q2 : STD_LOGIC_VECTOR (1 downto 0);
  signal q3 : STD_LOGIC_VECTOR (1 downto 0);

  --four latch outputs
  signal r1 : STD_LOGIC_VECTOR (3 downto 0);
  signal r2 : STD_LOGIC_VECTOR (3 downto 0);
  signal r3 : STD_LOGIC_VECTOR (3 downto 0);

  type s is array(7 downto 0) of std_logic_vector(5 downto 0);
  signal x : s := (others => "000000");

  component amm_module is
    Port( clk : in STD_LOGIC;
          a : in STD_LOGIC_VECTOR (3 downto 0);
          b : in STD_LOGIC_VECTOR (1 downto 0);
          c : in STD_LOGIC_VECTOR (3 downto 0);
          d : in STD_LOGIC_VECTOR (1 downto 0);
          p : out STD_LOGIC_VECTOR (5 downto 0));
  end component;

  component twolatch is
    Port ( Clk : in std_logic;
          p23 : in std_logic_vector(1 downto 0) := "00";
          o23 : out std_logic_vector(1 downto 0) := "00"
    );

```

```

    end component;

    component fourlatch is
        Port ( Clk : in STD_LOGIC;
              p23 : in STD_LOGIC_VECTOR(3 downto 0) := "0000";
              o23 : out STD_LOGIC_VECTOR(3 downto 0) := "0000");
    end component;

begin

    a1 <= a(3 downto 0);
    a2 <= a(7 downto 4);

    b1 <= b(1 downto 0);
    b2 <= b(3 downto 2);
    b3 <= b(5 downto 4);
    b4 <= b(7 downto 6);

--XL*Y10 (4x2 AMM)
MODULE1: amm_module port map (clk,a1,b1,c,d,x(0));

--XH*Y10 (4x2 AMM)
MODULE2: amm_module port map (clk,a2,b1,c,x(0)(5 downto 4),x(1));
mod1: twolatch port map(clk, x(0)(3 downto 2), q1);

--XL*Y32 (4x2 AMM)
MODULE3: amm_module port map (clk,a1,b2,(x(1)(1 downto 0) & q1),d,x(2));
mod2: fourlatch port map(clk, x(1)(5 downto 2), r1);

--XH*Y32 (4x2 AMM)
MODULE4: amm_module port map(clk,a2,b2,r1,x(2)(5 downto 4), x(3));
mod3: twolatch port map(clk, x(2)(3 downto 2), q2);

--XL*Y54 (4x2 AMM)
MODULE5: amm_module port map(clk,a1,b3,(x(3)(1 downto 0) & q2),d,x(4));
mod4: fourlatch port map(clk,x(3)(5 downto 2), r2);

--XH*Y54 (4x2 AMM)
MODULE6: amm_module port map(clk,a2,b3,r2,x(4)(5 downto 4), x(5));
mod5: twolatch port map(clk, x(4)(3 downto 2), q3);

--XL*Y76 (4x2 AMM)
MODULE7: amm_module port map(clk,a1,b4,(x(5)(1 downto 0) & q3),d,x(6));
mod6: fourlatch port map(clk, x(5)(5 downto 2), r3);

--XH*Y76 (4x2 AMM)
MODULE8: amm_module port map(clk,a2,b4,r3,x(6)(5 downto 4), x(7));

p <= (x(7) & x(6)(3 downto 0) & x(4)(1 downto 0) & x(2)(1 downto 0) & x(0)(1 downto 0));

end Behavioral;

```

## TESTBENCH

---

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

entity test is

end test;

architecture Behavioral of test is
    component ece689_proj is
        Port ( clk : in STD_LOGIC;
              a  : in STD_LOGIC_VECTOR (7 downto 0);
              b  : in STD_LOGIC_VECTOR (7 downto 0);
              p  : out STD_LOGIC_VECTOR (15 downto 0));
    end component;

    signal a : STD_LOGIC_VECTOR (7 downto 0);
    signal b : STD_LOGIC_VECTOR (7 downto 0);
    signal clk : STD_LOGIC := '0' ;
    constant period : time:= 1ns;
    signal p : STD_LOGIC_VECTOR(15 downto 0);

begin

    uut: ece689_proj port map(clk => clk,a => a, b => b,p => p);

    -- GENERATE CLOCK OF PERIOD = 1ns
    clk_process: process
    begin
        clk <= '0';
        wait for period/2;
        clk <= '1';
        wait for period/2;

    end process;

    -- INCREMENT A and B FROM
    test_process: process
    begin
        a <= "00000000";

        for i in 0 to 255 loop
            wait for 1ns;

            a <= std_logic_vector(unsigned(a) + 1);
            b<= "00000000";
            for j in 1 to 9 loop

                wait for 1ns;
                b <= std_logic_vector(unsigned(b) + 1);
            end loop;
        end loop;

        wait;

    end process;
end Behavioral;
```



## Results and Discussion:

### 1. Elaborated Design:

 


Figure 3: AMM

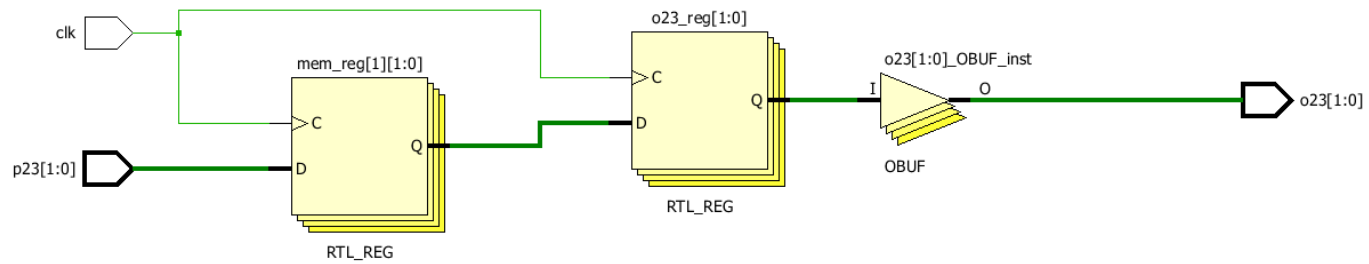


Figure 4: Two Latch

 


Figure 5: Four Latch

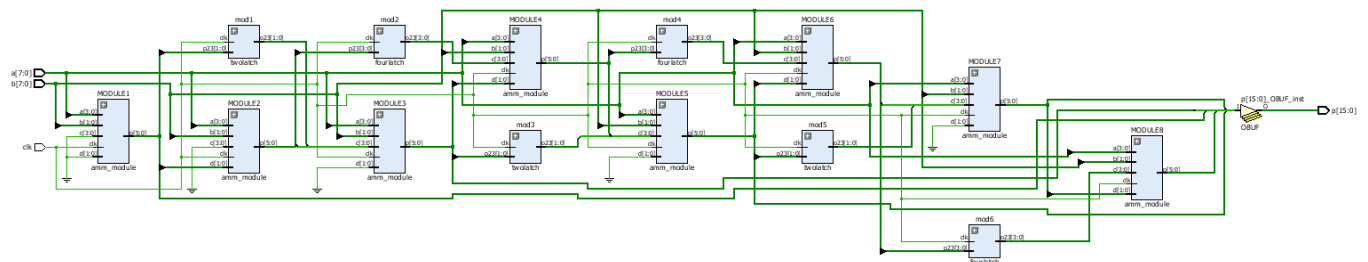


Figure 6: 8x8 Multiplication using 8, 4x2 AMM's

## 2. Project Summary:

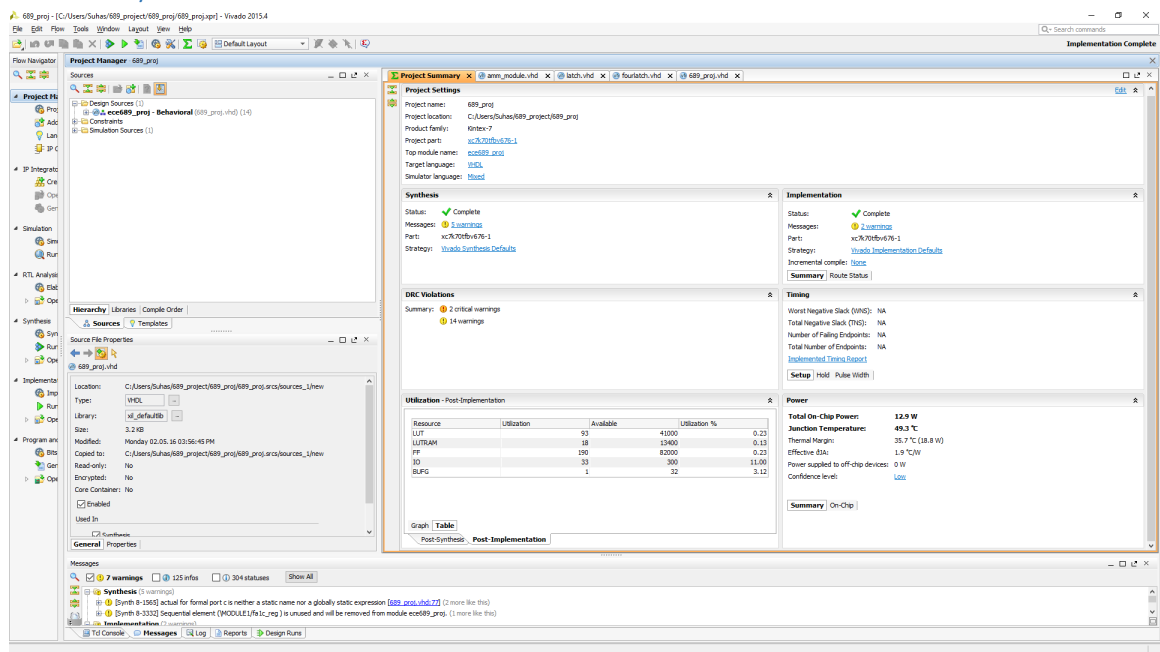


Figure 7: Project Summary

Resource	Utilization	Available	Utilization %
LUT	93	41000	0.23
LUTRAM	18	13400	0.13
FF	190	82000	0.23
IO	33	300	11.00
BUFG	1	32	3.12

Figure 8: Resource Utilization

 


Figure 9: Number of LUT's, IO's FF's etc used

### 3. Outputs:

#### Example 1.

A = 0C, B = 11;

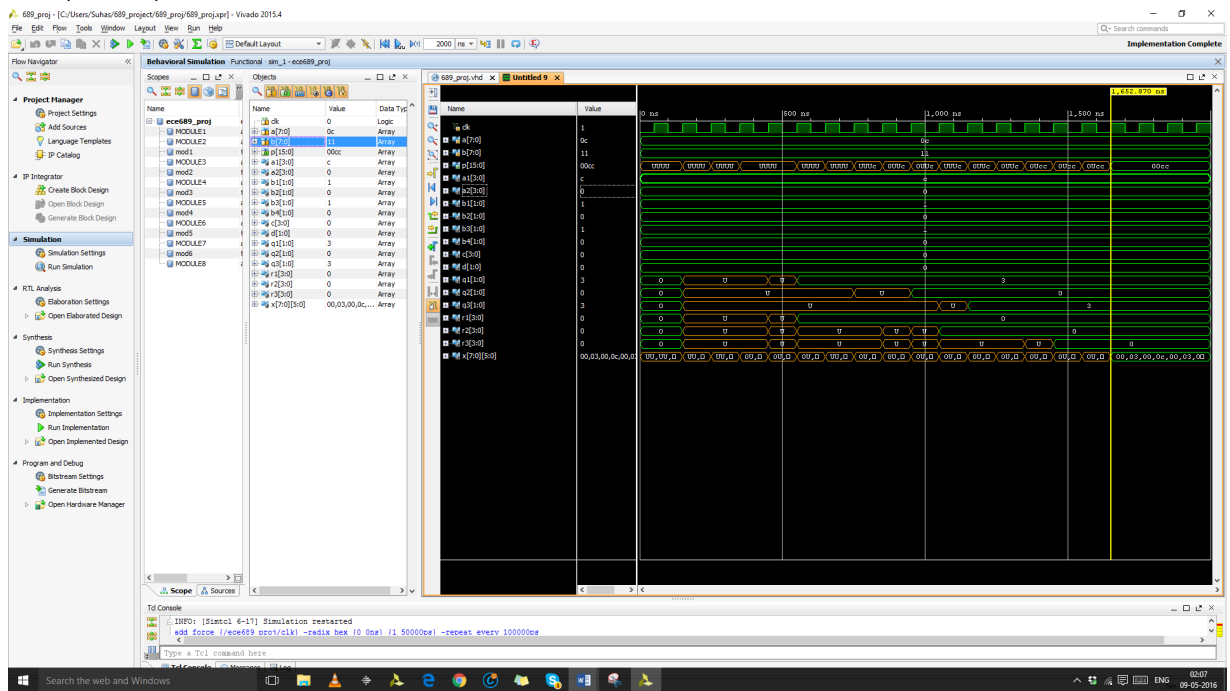


Figure 10: Example output#1

#### Example 2.

A = fa, B = 03;

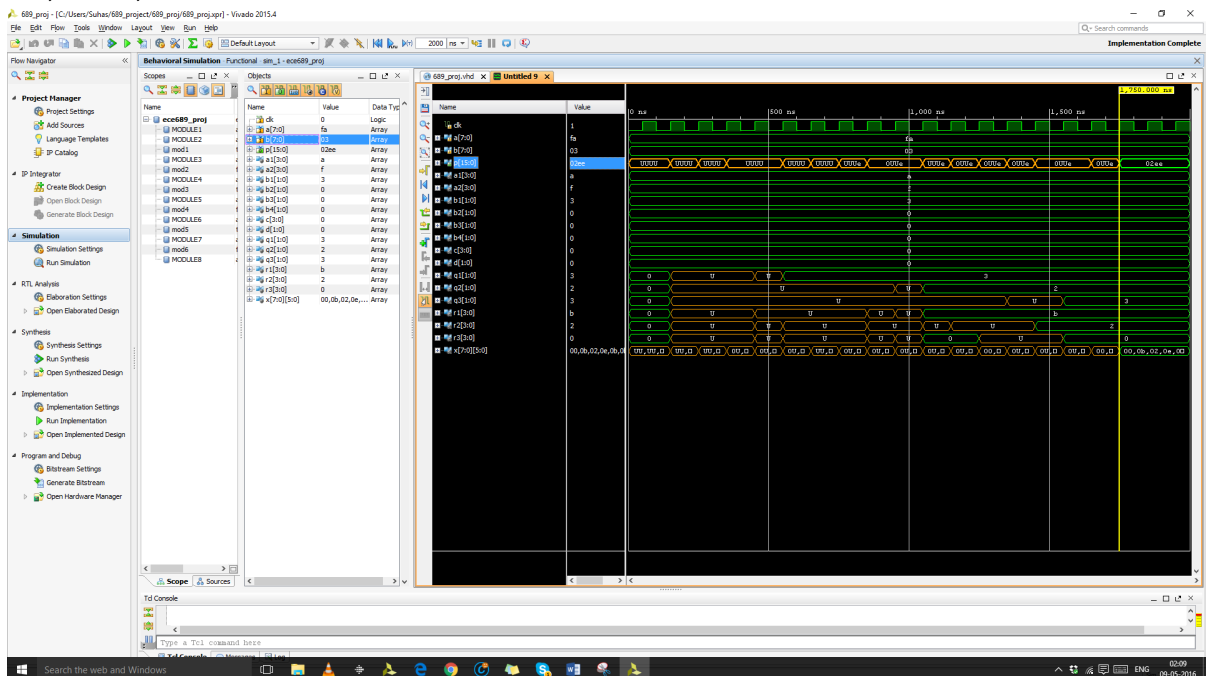


Figure 11: Example output#2

# POST BEHAVIORAL SYNTHESIS:

## 1. AMM

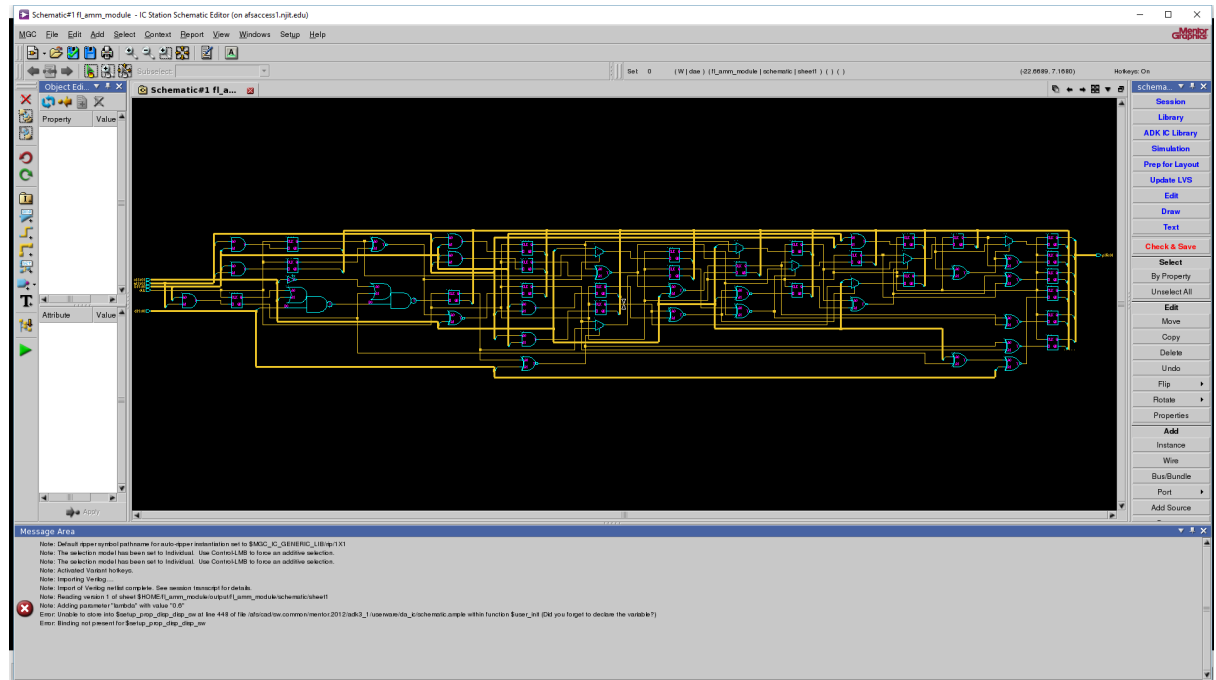


Figure 12: Schematic for AMM using Mentor Graphics toolkit

## 2. 8x8 multiplication

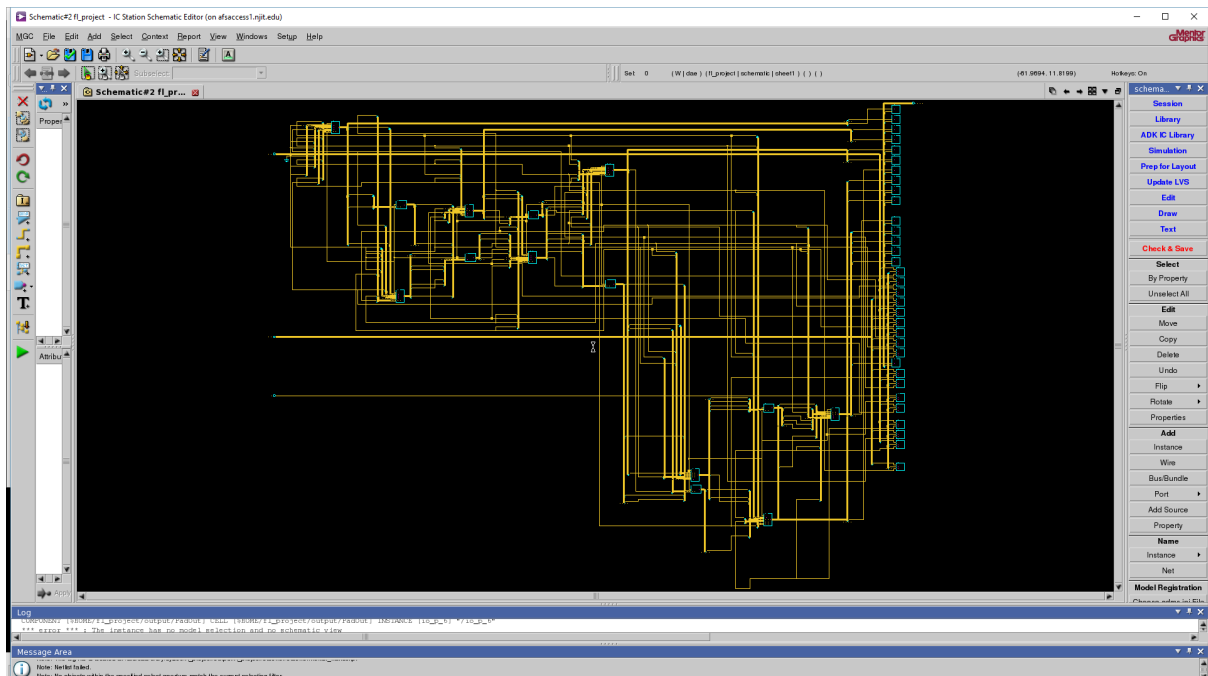


Figure 13: Schematic for 8x8 Pipelined Multiplier using 4x2 AMM's

### 3. Pad Frame

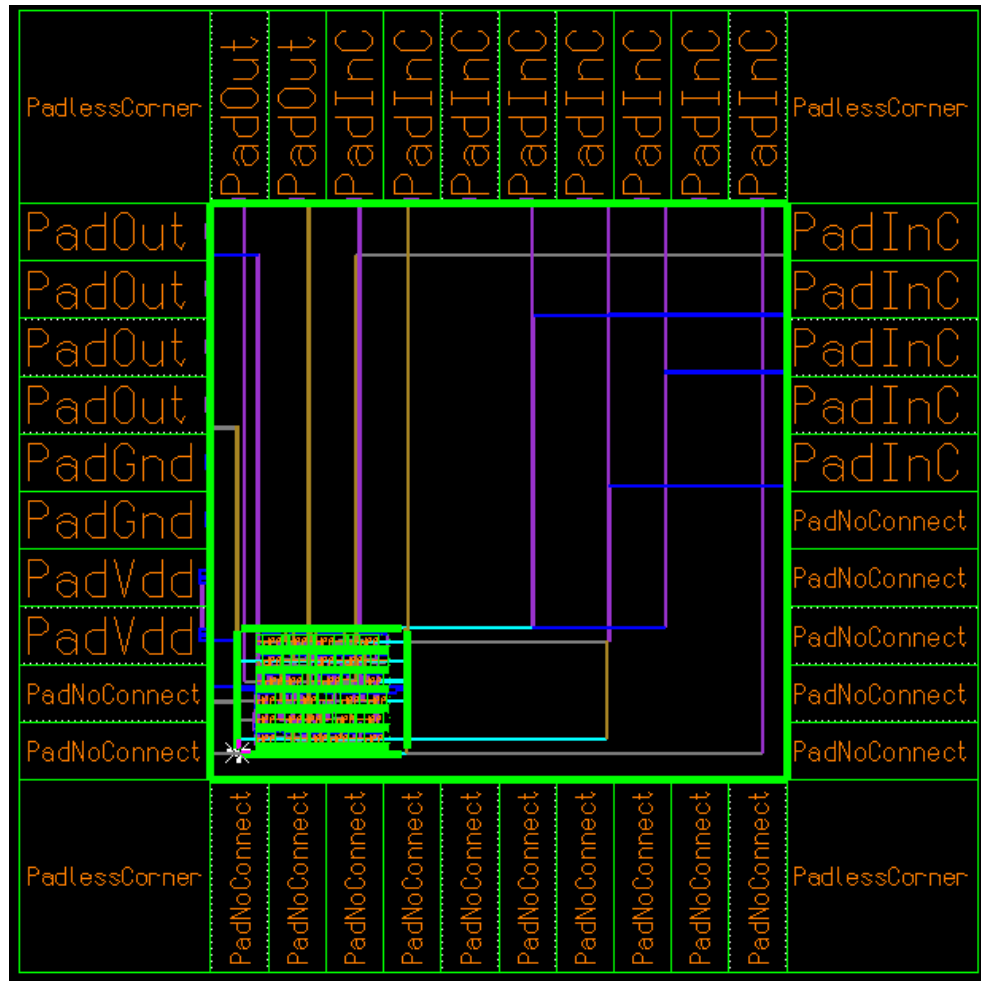


Figure 14: Pad frame for AMM

### 4. Layout for Two Latch

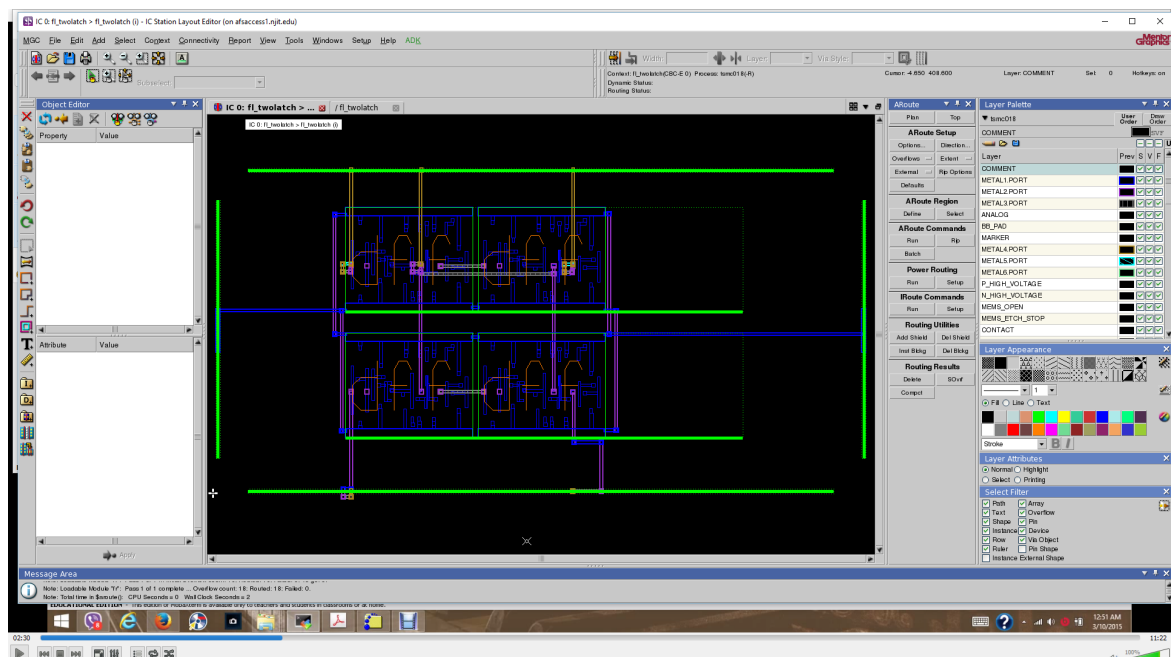


Figure 15: Layout of Two Latch

## 5. Schematic for Four Latch

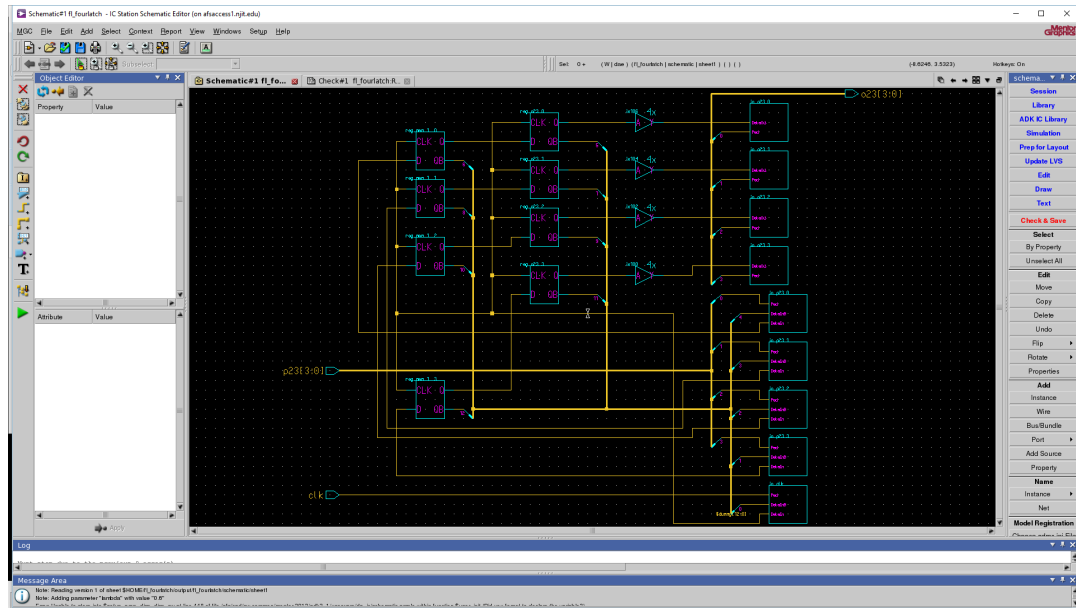


Figure 16: Schematic of Four Latch

## 6. Layout for Four Latch

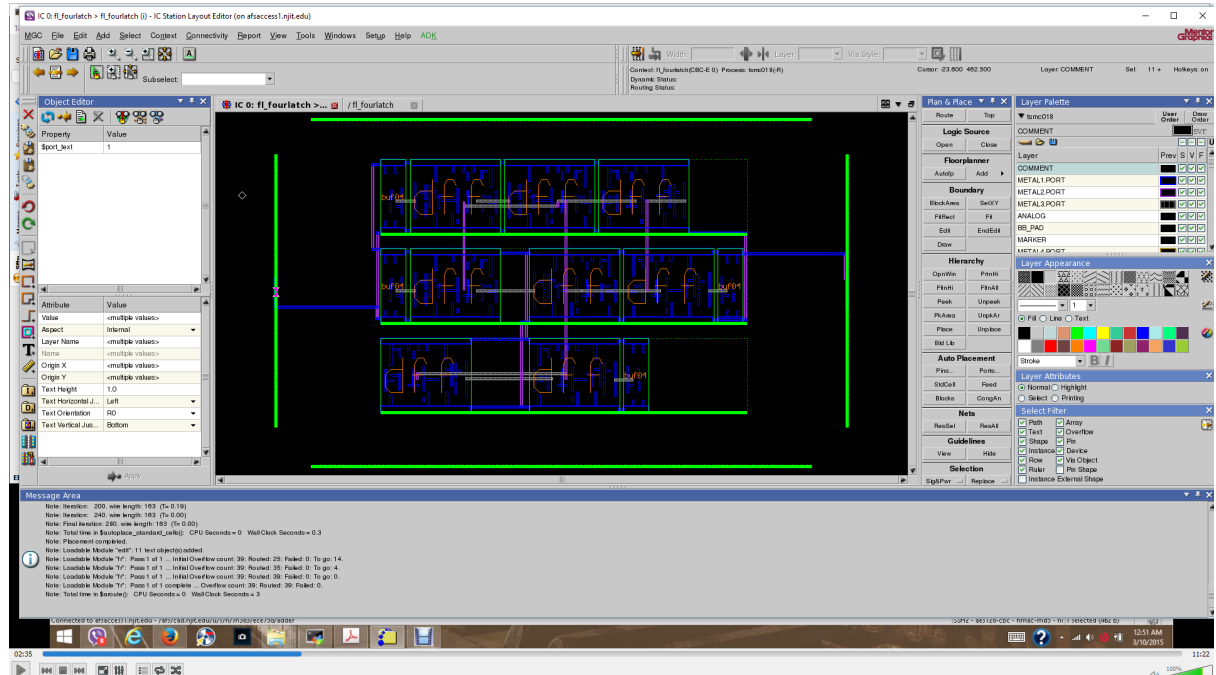


Figure 17: Layout of Four Latch